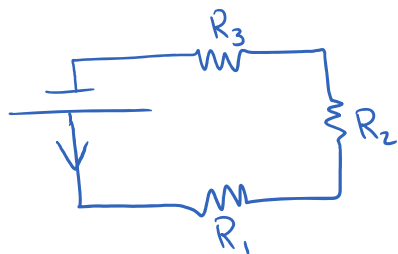


6.3 Kirchhoff's Laws

January 8, 2018 12:36 PM

$e^- \rightarrow$ energy - voltage
 \rightarrow motion - current

Series - the current flows through everything in circuit (no choice)
 - in series with the battery



$$V_s = V_1 + V_2 + V_3 + \dots = V_{AB}$$

total series voltage Terminal voltage

(e^- 's drop energy at each resistor in series)


$$I_s = I_1 = I_2 = I_3 = \dots$$

(all e^- 's go through everything in series)

$$R_s = R_1 + R_2 + R_3 + \dots$$

equivalent resistance in series

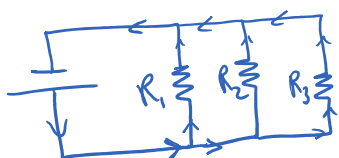Parallel - e^- 's have a choice of paths to follow
 - parallel w.r.t. the battery



$$V_p = V_1 = V_2 = V_3 = \dots = V_{AB}$$

parallel terminal voltage

(e^- 's divide btwn paths and drop the same energy at each resistor)

$$I_p = I_1 + I_2 + I_3 + \dots$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$\left(\begin{array}{l} \text{to solve} \\ \frac{1}{R_p} = \frac{x}{y} \\ R_p = \frac{y}{x} \end{array} \right)$$


Combined series and parallel
 - reduce it part by part.

Ex

I_0

5Ω I_0


① Series
 $5\Omega + 5\Omega = 10\Omega$

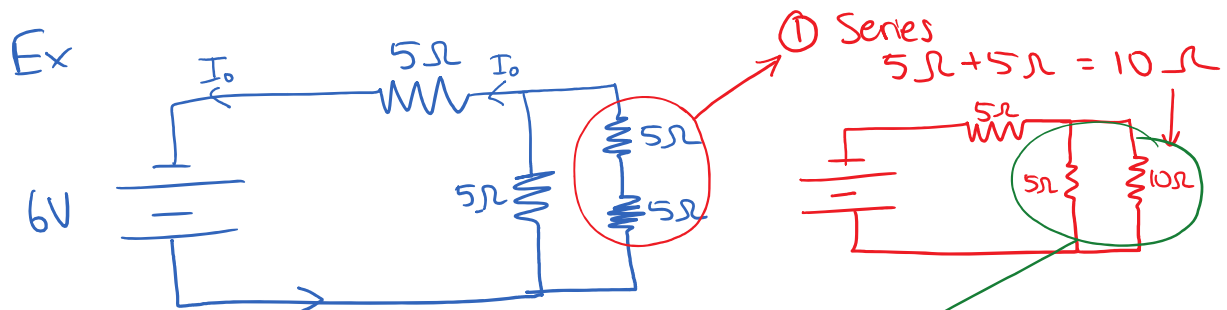

$I_o = ?$
 = total current out of battery
 $I_o = \frac{V_{AB}}{R_T} = \frac{6V}{?}$

② Parallel
 $\frac{1}{R_p} = \frac{1}{5} + \frac{1}{10} = \frac{2}{10} + \frac{1}{10} = \frac{3}{10}$
 $\frac{1}{R_p} = \frac{3}{10}$
 $\rightarrow R_p = \frac{10}{3} = 3.\bar{3}\Omega$

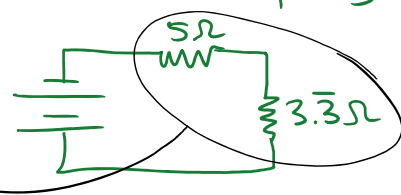③ Series
 $5\Omega + 3.\bar{3}\Omega$
 $= 8.\bar{3}\Omega = R_T$



④ $I_o = \frac{6V}{8.\bar{3}\Omega} = \underline{\underline{0.72A}}$

In Summary

Kirchhoff's Current Rule - the sum of all currents entering a junction equals the sum leaving.

Kirchhoff's Voltage Rule - the sum of all voltage drops of one e^- around the circuit equals the terminal voltage put into the circuit.

Practice pg 245 #1-2
 pg 246 #1-4
 Worksheet #1-7